

Index

A

AAF. *See* Antialiasing filter.
Accumulate-and-dump circuit, 129, 132
Accumulator, 19, 129, 134, 235-236
Accuracy, 195, 200, 269
Active-RC Integrator, 73, 75,
 filter, 80, 82-83, 87-88, 97-98, 101, 103-106,
 109, 112, 116
Adaptive filtering, 93
ADC. *See* Analog-to-digital converter.
Adder, 94, 126, 145, 147, 151, 156, 158-159, 273,
 309, 320, 322
Aliasing, 21, 27-72, 93, 127-129, 140, 143-144,
 306, 317
 quantization noise, 169
Amplitude modulation, 187, 207, 285, 288, 315
Analog RC filter, 80, 82-83, 87-88, 97-98, 101,
 103-106, 109, 112, 116
Analog Sinc averaging filter, 10-11
Analog-to-digital converter (ADC), 21, 27, 94,
 164-224, 225-284
 1-bit, 236
 bandpass, 134, 287-300
 gain, 246
 high-speed, 301-324
 Nyquist-rate, 43, 63, 220-225, 241, 306-308
 pipeline, 38
 SPICE models for, 119-123, 160, 176
Antenna, 292
Antialiasing filter (AAF), 27-40, 73, 93, 139, 144,
 198-199, 203, 205-206, 302
Aperture jitter, 179, 202, 317
Autocorrelation function (ACF), 183
Autozeroing, 57-58, 62, 71
Average power, 183-187, 198
Average value, 44, 168, 183-187, 200, 212, 244,
 315
Averaging,
 bandpass filter, 19, 134-139, 160, 290-292
 clock jitter, 198
 decimation, 209-211
 filter, 13-14, 126, 131, 133-134, 201, 220, 223,
 234, 239-241, 266-267
 highpass filter, 19, 129, 134
 improving signal-to-noise ratio (SNR), 13,
 190-194

Averaging (continued),
 interpolating filter, 43-50, 71, 139-142, 199,
 235, 273
 limiting bandwidth, 13-14
 linearity requirements, 194-195
 noise, 250
 quantization noise, 202, 211
 without decimation, 132-133

B

B, bandwidth of the input signal, 129-130, 133-134,
 182, 198-199, 208-209, 212, 220, 229,
 237-241, 248, 250, 267, 285, 290, 296, 324
B device. *See* Nonlinear-dependent source.
Bandpass filter, 19, 96, 103-111, 129, 134-139, 160
Bandpass modulators, 263, 285-298, 301, 324
Bennett's criteria, 165-166
Bilinear transfer function, 95
Binary offset, 123-125, 204-205, 274
Biquad filters, 73, 99-101
Biquadratic transfer function, 99
Bottom plate of a capacitor, 67
Bottom plate sampling, 39-40, 54, 219

C

CAI, *See* continuous-time analog integrator.
Calibration, 322
Canonic digital filter, *See* Digital filter.
Capacitance,
 bottom plate, 54
 input, 86, 93, 247, 282, 319
 load, 88-89
 noise calculation, 307
 parasitic, 66, 69, 83-84, 219, 279-281
Capacitive feedthrough, 39, 251, 257
Cascade of integrators and combs filters (CIC
 filters), 142
Cascaded modulators, 233, 264, 275-280
Charge injection, 39-40, 251, 257, 294
Charge pump, 120
Chopper stabilization, 71
CIC filters, *see* Cascade of integrators and combs
 filters
Clock generation, 53, 316-318
Clock jitter, 178-189
Coherent sampling, 175-176, 202
Comb filter, 8-21, 25, 129-131, 133-143, 224
Common-mode feedback (CMFB), 60-61, 88-89
Common-mode rejection ratio (CMRR), 87, 252
Common-mode voltage, $V_{CM} = 500$ mV in this book
Comparator,
 clocked, 163, 319-320
 gain, 244-246, 259, 262-263, 295
 hysteresis, 246-247

Comparator (continued),
 LSB, 204
 noise, 163, 246-247, 250
 offset, 246-247
 placement, 261
 Constant delay, 10, 31, 145, 171
 Continuous-time analog integrator (CAI), 73, 75, 95
 Continuous-time comb filter, 10-11
 Continuous-time Fourier transform, 23
 Convolution, 35, 175
 Correlated double sampling (CDS), 59, 66, 71
 Cosine window. *See* Hanning window.
 Counter, 45, 126-129, 130, 270-271

D

DAC. *See* Digital-to-analog converter.
 DAI. *See* Discrete analog integrator.
 dBc (decibels with respect to the carrier), 177, 189
 Dead zones, 215, 217, 232
 Decimation, 33-34, 127-129, 132, 222-223,
 306-312, 321-322
 bandwidth limitations, 34
 decimating filter, 143-144, 157, 203, 239
 Delta modulation, 199
 Delta-sigma modulation, 199, 233-234 *See*
 noise-shaping.
 Demodulator, 199-200, 235-236, 271-272
 Diff-amp, 61, 86, 89, 222
 Differentiator, 14-15, 119, 275-276
 Digital averaging filter, 192, 220
 Digital comb filter, 11-18
 Digital filter, 119-162
 biquad, 155-159
 canonic, 151-155
 finite impulse response (FIR), 133-134,
 145-146, 161
 infinite impulse response (IIR), 134
 stability, 146-147
 Digital integrator, 19-21, 235
 Digital I/Q extraction to baseband, 297-298
 Digital resonator, 134-139, 160
 Digital signal processing (DSP), 27, 32, 203
 Digital-to-analog converter (DAC), 69, 119-123,
 204-205, 213-214, 235-236, 272-275
 Dirac delta impulse, 23, 28
 Discrete analog integrator (DAI), 66-70, 90-93,
 233, 251, 260
 Discrete-time integrator, 90-95
 Distortion, 35, 37, 49, 65, 71, 176-178, 187,
 206-208, 213-214, 225-226, 249, 251-252, 269,
 273, 288-289
 Dither, 166, 195-198, 242, 282
 Droop, 37, 39-41, 47-48, 127, 129, 132, 142, 157,
 209, 212, 223, 241, 267
 DSP. *See* Digital signal processing.
 Dynamic range, 83, 177, 251, 276, 279

E

Effective number of bits, N_{eff} , 173, 176, 179,
 181-182, 188, 202
 Error feedback, 235, 271-275, 283
 Expected value, 186

F

Feedback gains in a DAI, 260
 Filters,
 active-RC, 75
 accumulate and dump, 129
 bandpass, 19, 96, 103-111, 129, 134-139, 160
 bilinear, 95
 biquad, 73, 99-101
 comb filter, 8-21, 25, 129-131, 133-143, 224
 decimating filters, 143-144, 157, 203, 239
 digital. *See* Digital filter.
 exact frequency response of discrete-time filter,
 94
 finite impulse response (FIR), 133-134,
 145-146, 161
 g_m -C filters. *See* transconductor-C filter.
 highpass, 19, 129, 134
 in a higher-order modulator, 267
 infinite impulse response (IIR), 134
 integrating filters, 73-118
 interpolating filters, 139-142
 ladder filter, 117-118
 lowpass, 75
 MOSFET-C, 83
 Q peaking and instability, 112
 Sinc, 133
 SNR, 82-83, 87
 stability in digital filters, 146
 switched-capacitor, 90-95
 transconductor-C filter, 97
 tuning, 80, 83, 86, 93, 98
 Finite impulse response (FIR) filter, 133-134,
 145-146, 161
 Finite op-amp gain-bandwidth product, 55-57,
 78-79
 First-order noise shaping, 208, 210, 224, 233, 238,
 254
 FIR. *See* Finite impulse response.
 Forward modulator gain, 243
 Fourier series, 23
 Fourier transform, 24

G

Gain error term, 176-177, 204, 213-214, 219,
 247-249, 280
 g_m -C (transconductor-C) integrators, 86-90
 Gaussian probability distribution, 187, 197

H

Hanning window, 175
 Harmonics,
 square wave, 189
 High-frequency transistor, 89-90
 Highpass filter, 19, 129, 134
 Higher order modulators, 267
 Hold register, 46-50
 Hysteresis, 246-247

I

I, in phase or real component, 4-6, 285-286,
 297-299
 IIR. *See* Infinite impulse response filter.
 Impulse sampling, 28-31
 Infinite impulse response (IIR) filter, 134
 Integrator,
 analog. *See* Continuous-time analog integrator.
 digital, 19-21, 235
 discrete analog integrator (DAI), 66-70, 90-93,
 233, 251
 gain, 113, 244-246, 248, 255, 257-260, 264,
 276, 303
 leakage, 247-248, 282
 Interpolation, 32, 43-46, 48-50, 71, 139-142, 235,
 273
 Interpolative modulators, 271-272
 Inverse Fourier transform, 23

J

Jitter. *See* Clock jitter.

K

K, oversampling ratio, averaging factor, or
 interpolation increase, 33, 43-50
 clock jitter, 181-182
 K-Delta-1-Sigma, xvi, 222, 303-304, 320-324
 K-path, K_{path} , 50-53, 220-224, 228, 230, 301-302,
 317

L

Ladder filter, 117-118
 Least significant bit (LSB), 119, 204
 Limit cycle oscillations, 241, 315
 Linear phase, 25, 30-31, 145
 Linearity, 212, 214
 Linearity requirements for averaging, 191-195
 Lowpass filters, 73-74
 LSB. *See* Least significant bit.

M

MASH modulator. *See* Noise-shaping
 Matching, 53, 55, 94, 200, 211, 212, 230, 279, 323
 Matlab, 171
 Mean, 186
 Miller integrator, 75
 Mixed-signal system block diagram, 27
 Modulation noise, 206-208, 212, 237
 Modulator,
 bandpass, 287-297
 cascaded, 275
 first-order, 233
 gain, 243
 higher-order, 265-269
 interpolative, 271-272
 multibit, 269
 noise-shaping, 199-201, 233
 predictive, 200
 second-order, 253
 MOSFET-C Integrators, 83-85
 Multibit modulators, 269
 Multiplexer (MUX), 236, 297
 Multipliers, 34, 64, 94, 291, 297-298
 Multistage noise shaping modulator (MASH), 275
 MUX. *See* Multiplexer.

N

Noise,
 averaging, 190
 clock jitter,
 correlated double sampling (CDS), 59, 66, 71
 modulation, 206-208, 212
 quantization noise, *See* Quantization noise.
 Noise transfer function (NTF), 200-201, 205-208,
 224, 233, 253-254
 Noise-shaping (NS), 199-201, 233, 253
 Non-overlapping clock generation, 51, 53, 304, 317
 Nonrecursive filters, 133
 Number representation, 123-126
 Nyquist,
 differences between noise-shaping converters,
 241
 frequency, 17, 21, 27, 29, 31, 37-40
 rate ADC, 43, 63, 220-225, 241, 306-308

O

Offset,
 autozero, 57-59, 62
 comparator, 221-222, 224, 246
 DAC, 214
 op-amp, 54-55, 58-62, 66, 72, 212, 247-250
 Offset binary format, 123-125, 204-205, 274

Overflow, 124-126, 143, 145-148, 211, 214-215, 221, 273
 Oversampling,
 Oversampling ratio. *See* K, oversampling ratio
 or averaging factor.

P

Passive noise-shaping, 205-207, 216-219
 Path settling time, 302
 Pattern noise, 241
 PDF, probability density function, 185
 average value (mean or expected value), 186
 Gaussian, 186-187, 197-198
 standard deviation, 186
 variance, 186
 Phase-delay relationship, 4
 Phase,
 discrete analog integrator (DAI),
 digital filter, 10-11, 13-15, 17-21, 130, 151
 linear, 9, 30-31, 145, 171
 noise, 188-189
 response, 76, 79-81, 88, 104
 shift, 4-5, 8, 95-96, 141
 Phase-locked loop, 180
 Pipeline ADC, 38, 122, 176, 220, 307
 PLL. *See* Phase-locked loop.
 Power
 average, 183-184, 186-187
 Power spectral density (PSD), 166, 172, 183, 188,
 190, 193
 jitter, 186-189, 198
 quantization noise, 166, 168, 193
 Predictive coder. *See* Predictive modulator.
 Predictive modulator, 199-200
 Probability density function, *See* PDF.
 PSD. *See* Power spectral density.

Q

Q (pole quality factor), 99-106
 high Q, 107-114, 117
 peaking and instability, 112-113
 QAM, *See* Quadrature amplitude modulation.
 Quadrature amplitude modulation, 285
 Quadrature or imaginary component, 4-6, 285-290,
 297-299
 Quantization noise, 122, 163-178, 185-196, 211,
 224, 233-234, 237, 240, 242-243, 251, 253,
 266, 273-276, 279, 312-314
 Quantize, 33
 Quantizer, 43, 125, 163-164, 203-204, 235-239,
 269, 271-274, 314

R

Random signals, 185, 196, 216
 quantization noise, 168-169
 spectral density, 190
 standard deviation, 186
 variance, 186
 RCF. *See* Reconstruction filter.
 Reconstruction filter (RCF), 27, 29, 32, 39, 87, 166,
 139, 185, 187, 235, 273
 Resolution, 13, 56-57, 83, 176, 191, 194-195,
 199-200, 203, 209-210, 215, 230, 237-240,
 253-254, 265, 269, 273, 306-307, 322
 loss because of jitter, 178-181
 Return-to-zero (RZ), 35, 37, 39, 42
 Ripple, 241-242, 282, 288-289
 RMS quantization noise voltage, 166, 168-170, 211,
 237, 249, 253, 266-267
 calculating from a spectrum, 185, 187, 193
 Root mean square (RMS) voltage, 168
 RZ. *See* Return-to-zero.

S

Sample and hold (S/H), 27, 35-43, 54-66
 matching of the capacitors used,
 single-ended to differential, 65
 subtraction, 63
 Sample frequency reduction. *See* Decimation.
 Sampler, 28-35
 Sampling and Aliasing,
 coherent. *See* coherent sampling.
 Sampling gate, 28
 Second-order noise-shaping, 227-229, 253
 Settling time, 57, 60-61, 221, 248-249, 302
 SFDR. *See* Spurious-free-dynamic range.
 SFFM. *See* Single frequency frequency modulation.
 S/H. *See* Sample and hold.
 Side lobes, 47-48
 Sigma-delta modulation, *See* noise-shaping
 Signal-to-noise and distortion ratio (SINAD). *See*
 Signal-to-noise plus distortion ratio (SNDR).
 Signal-to-noise plus distortion ratio (SNDR), 93,
 176-178, 187, 197, 202
 Signal-to-noise ratio (SNR), 70, 82-83, 87, 137,
 163-202, 208-229, 238-242, 247-248, 250-253,
 265
 Signal transfer function (STF), 200-201, 205-206
 Sinc filter, *See* digital averaging filter.
 Sinc function, 32, 36-39, 47-49
 Sinc-shaped digital filter, 126-144
 Slew-rate, 57, 179, 248-249
 Smoothing filter, *See* reconstruction filter.
 SNR. *See* Signal-to-noise ratio.
 SNDR. *See* Signal-to-noise plus distortion ratio.
 Spike, 177

Spurious free dynamic range (SFDR), 177, 242
 Squarewave, 22, 25, 126-128, 166, 175
 Stability,
 digital filter, 146
 filter, 112
 noise-shaping modulator, 258-264, 269, 275,
 293
 Standard deviation, 186, 198
 Subtraction, 63, 126, 271
 Switched-capacitor filters, 91-95, 98-99, 106-111
 Switches,
 capacitive feedthrough, 39, 251
 charge injection, 39-40, 251, 257, 294
 MOSFET, 318

T

Taylor series, 6
 T/H, *See* Track-and-hold.
 Thermometer code, 308
 Time-domain description of reconstruction, 31-33
 Time-interleaved ADC, 220-222, 232, 313, 323
 Track-and-hold, 41-43
 Transconductor-C filters, 86
 bilinear, 97
 biquad, 114
 Triangular response, 133
 Tuning, 80, 83, 86
 orthogonal tuning, 98
 Two's complement, 123-126, 131, 137, 147,
 204-205
 subtraction, 126

U

Unit step function. *See* $u(t)$.
 $u(t)$, 35-36

V

Variance, 168, 186
 V_{CM} , ($V_{DD}/2$ or 0.5 V in this book)
 V_{DD} , (1.0 V in this book)
 Von Hann window. *See* Hanning window.

W

White noise, 169, 172, 269
 Windowing, 175-176
 Wireless, 285, 291
 I/Q extraction, 297-298

Z

z
 defined, 7, 12
 domain, 6-8
 to s-transform (practical), 51, 149
 z -plane, 7, 15
 Zero-Order Hold (ZOH), 27
 Zero padding, 44-45